

Final Exam

1

Question: 1

(a) Comparison between FET and BJTs

→ FETs ←


- the FET is a unipolar device, which depends on only one type of charge carriers, either electrons or holes, or by other mean, the current is conducted by one type of charge carriers flowing through one type of S.C.
- the FET is voltage controlled, i.e. an i/p voltage controls an o/p current
- the i/p impedance is extremely high (MΩ) and therefore they require very little power from the driving source (so they are preferred over BJTs)
- the FET is simpler to fabricate and occupies less space in integrated form (so they are preferred over BJT to be used in integrated form)

→ BJTs ←


- the BJT is a bipolar device, which depends on both types of charge carriers
- the BJT is current controlled, i.e. an i/p current controls an o/p current
- the i/p impedance is smaller than FET
- the BJT occupies a larger space in integrated form

(2)

 (b) For a JFET, the channel gate p-n Junction is reverse biased so that the current is prevented to flow in the gate terminal.



 For a MOSFET (either D-MOSFET or E-MOSFET) the gate is insulated from the channel, so that the current is prevented to flow in the gate terminal.



(c) At $V_{GS} = 0V$

$$V_{DS}(P) = V_{GS} - V_P$$

$$\therefore V_P = -4V$$

$$I_{DSS} = 16mA$$

$$V_{GS(off)} = V_P = -4V$$

At $V_{GS} = -2V$

$$V_{DS}(P) = V_{GS} - V_P$$

$$4 = -2 - V_P$$

$$V_P = -6V = V_{GS(off)}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\therefore 16 = I_{DSS} \left(1 - \frac{-2}{-6}\right)^2$$

$$\therefore I_{DSS} = 36mA$$

3

3

$$V_{GS} = 2V$$

$$V_{DS(P)} = V_{GS} - V_P$$


$$4 = 2 - V_P$$

$$V_P = -2V = V_{GS(off)}$$


$$16 = I_{DSS} \left(1 - \frac{2}{-2} \right)^2$$

$$I_{DSS} = 4mA$$


(ii) case (A)

 

case (B)

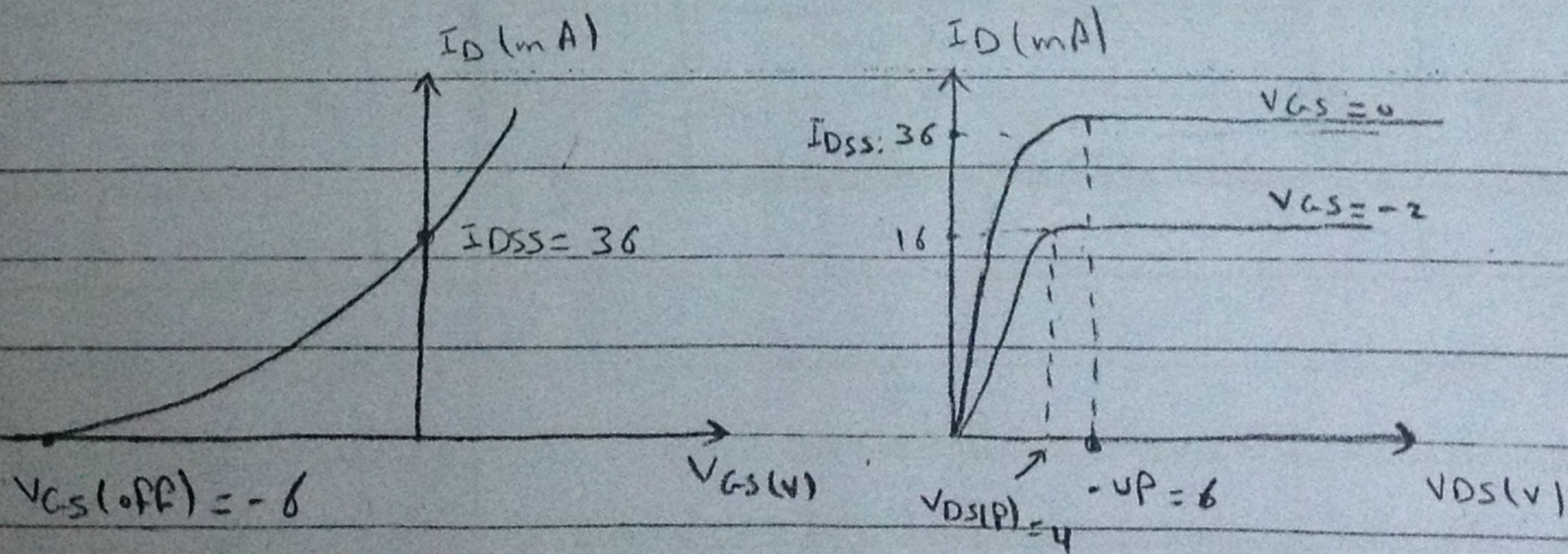

case (C)

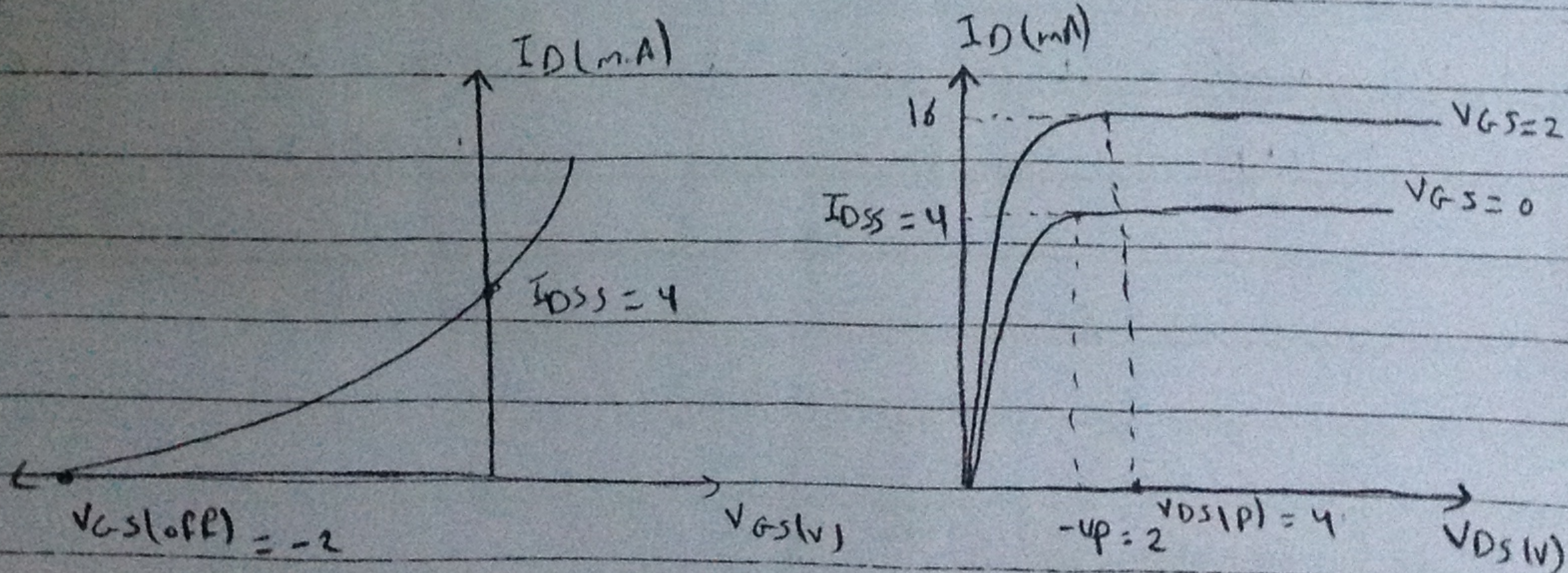


(4)

(iii) I_{Dss} is the saturation current passes through the channel when $V_{GS} = 0$ and $V_{DS} = -V_p$

V_p is the value of V_{DS} at which the channel is pinched off at the drain end only when $V_{GS} = 0$ and the current is I_{Dss}

$V_{GS(off)}$ is the value of V_{GS} at which the channel is completely pinched off and is entirely depleted of charge carriers, hence no current will flow ($I_D = 0$)

V_p

 


* $V_{GS} = 0$

* $I_D = I_{Dss}$

* the channel is pinched off at drain end only

$V_{GS(off)}$

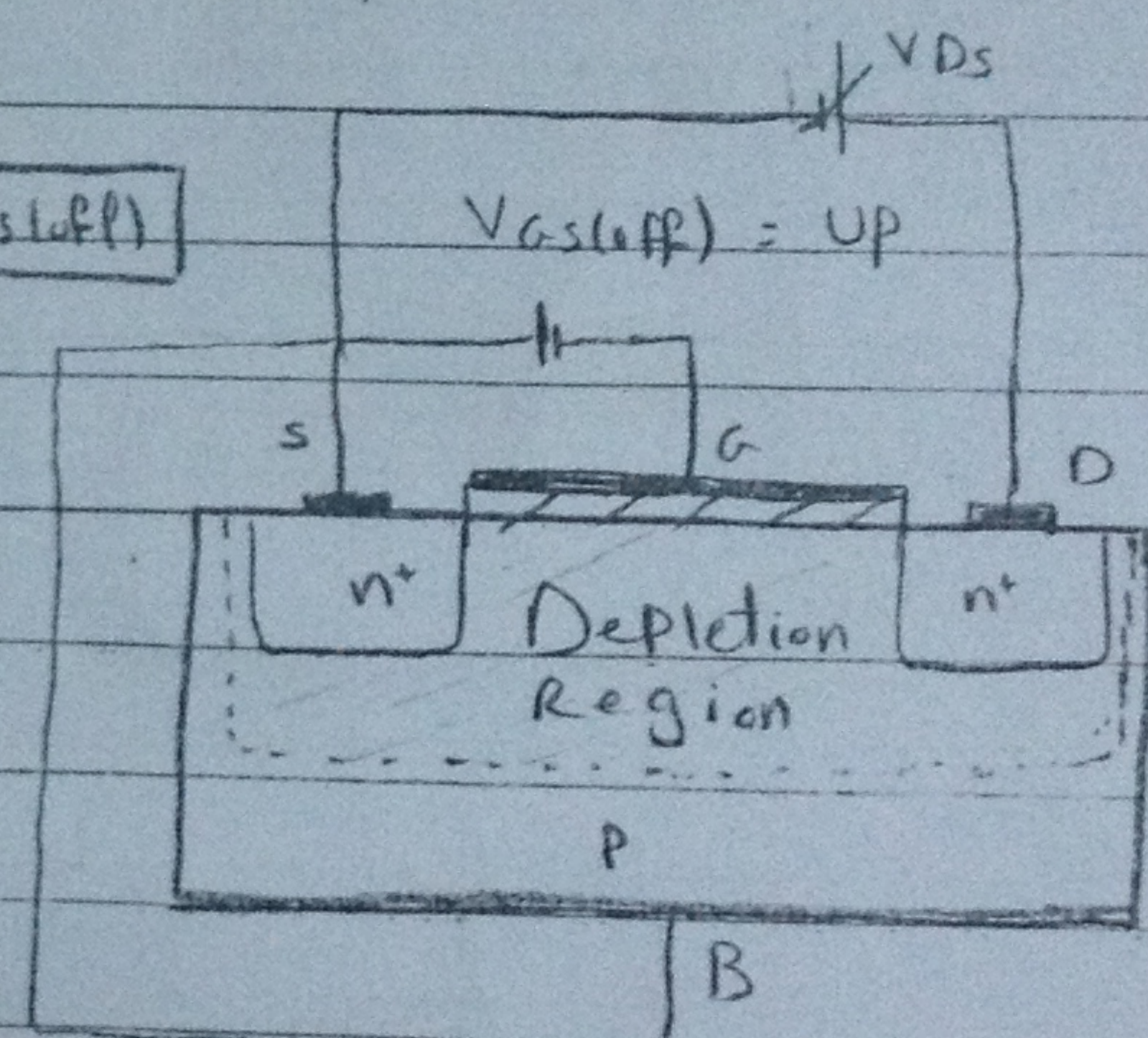

* $V_{GS(off)} = V_p$

* $I_D = 0$

* the channel is completely pinched off

5

5


Question: 2

(a) (i) the FET is E-MosFET

and the drain current does not flow because $V_{GS} < V_t$

 (ii) steps:

- * at the beginning, when +ve voltage on the gate deposits +ve charges on the metal and calls for a corresponding net -ve charge at the surface of the s.c., such a -ve charge in a p-type material arises from depletion of the holes from the region near the surface




these holes are pushed downward into the substrate, leaving behind a carrier depletion region

- * (if V_{GS} is made more +ve), this will attract more electrons from the n^+ source and drain regions into the surface of the substrate under gate

when a sufficient number of electrons accumulates in the channel region, an n region is induced connecting source and drain region

 
- * this value of V_{GS} is called (V_t) and it must be exceeded for current I_D to flow through the induced channel



(6)

 (iii) Transfer ch/cs

V_t : the value of V_{GS} at which a sufficient number of mobile electrons accumulate in the channel region to form a conducting channel



(b)

(i) $V_{GS} = 2V$, $V_{DG} \gg 12V$, the volt across R_D is $9V$

$$I_D = \frac{V_{RD}}{R_D} = \frac{9}{1} = 9mA$$

For $V_{DG} \gg 12V$, I_D is const at $9mA$

$$V_P = -12V$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$


$$9 = I_{DSS} \left(1 - \frac{-2}{-12}\right)^2$$

$$\therefore I_{DSS} = 12.96mA$$

$$V_{GS(off)} = V_P = -12V$$

(ii) R_G is taken large to isolate the gate from ground for ac signals

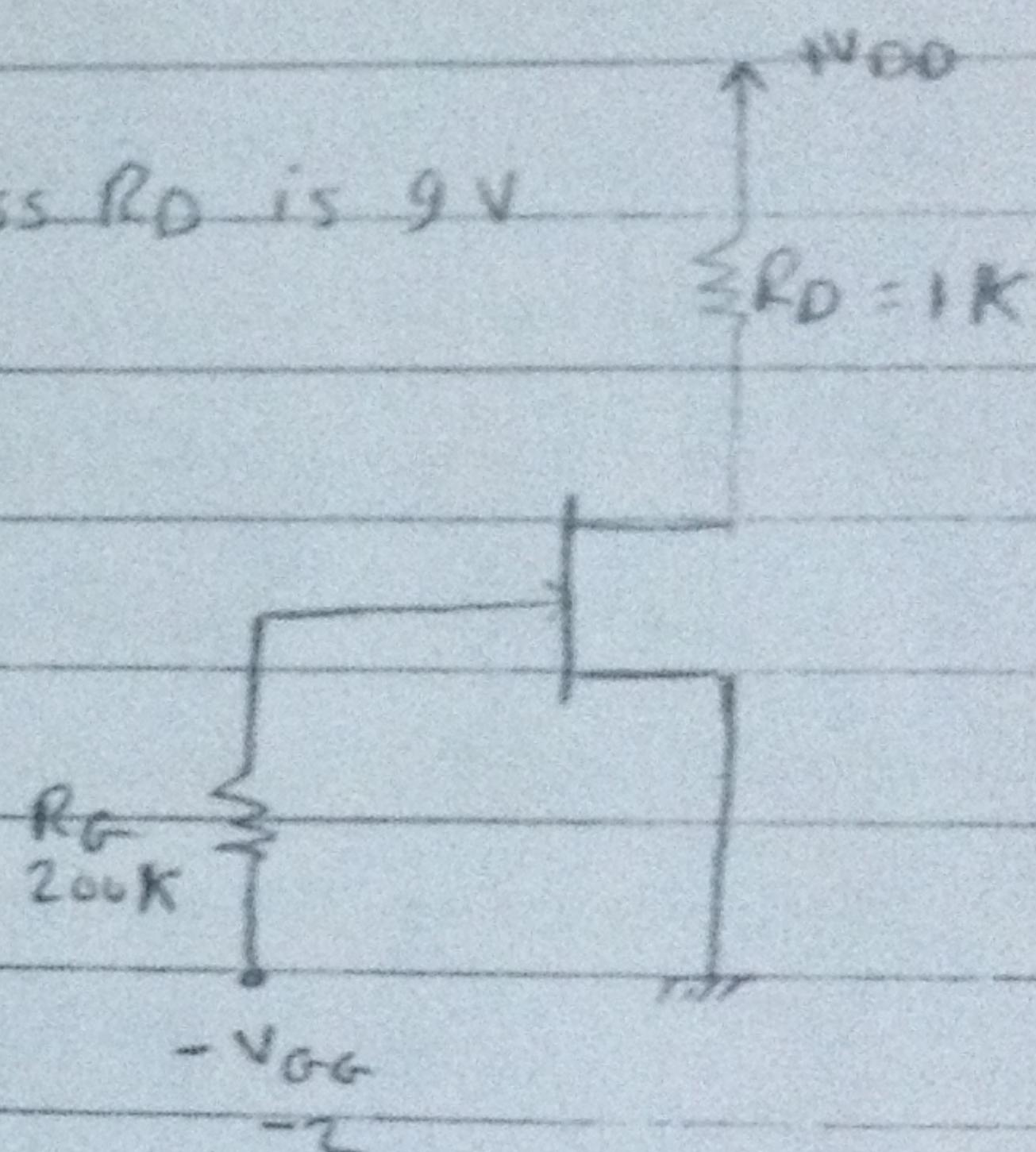(iii) this type of biasing can be used to bias all types of FET because it provide the appropriate value of V_{GS} , but with E-MosFET we must connect the gate terminal with the +ve polarity of the V_{GG} source




(14)

1

it is not preferable to use this technique for biasing FETs because it is not a stable biasing technique, since the characteristics of the individual FETs used in mass production may vary over a wide range, thus for some circuits, the amount of V_{GS} may provide a very large drain current, whereas in other circuits the same value of V_{GS} might reduce the drain current to near zero.

* a preferable biasing technique is (Voltage divider Bias)

 this technique is a stable one as it minimizes the variance in I_D between different FET devices.



* For JFET and N-MOSFET:

R_S is a self-bias resistance and also acting as feedback resistance.

but for E-MOSFET:

R_S is not self-bias resistance and its role is to provide negative feedback that stabilizes the DC operating point.

8


Question 3

(a) FET applications:

* analog application:

Analog switch

 When no gate voltage is applied to the FET i.e. $V_{GS} = 0$, the FET becomes saturated and behave like a small resistance usually of value less than 100Ω and o/p voltage.



$V_{out} =$

$$\frac{R_{DS(on)}}{R_D + R_{DS(on)}} V_{in}$$

since $R_D \gg R_{DS(on)}$, so V_{out} can be taken equal to zero



When a -ve voltage equal to $V_G(off)$ is applied to the gate, the FET operates in the cut-off region and acts as a very high resistance usually of some mega ohm, hence the o/p voltage becomes equal to input voltage

* digital applications *

CMOS Inverter

When a High is applied to the input, Q_1 is off and Q_2 is on, this condition connects the off to ground through the on resistance of Q_2 resulting in a Low o/p

 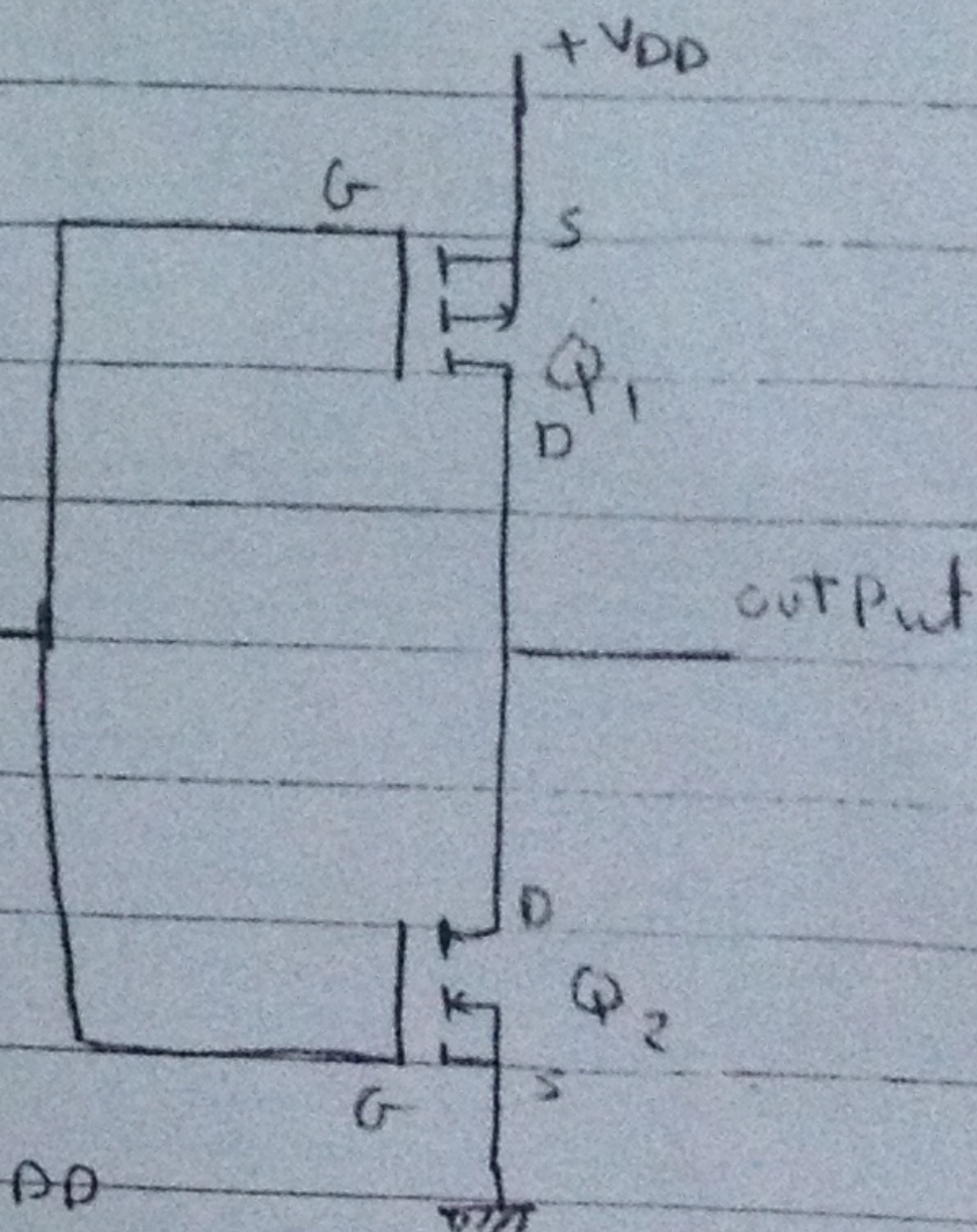
When a Low is applied to the i/p, Q_1 is on and Q_2 is off, this condition connects the o/p to $+V_{DD}$ through the on resistance of Q_1 resulting in a high o/p



~~at C_{gs} and C_{gd} for a JFET~~

~~\times C_{gs} and C_{gd}~~

(9)

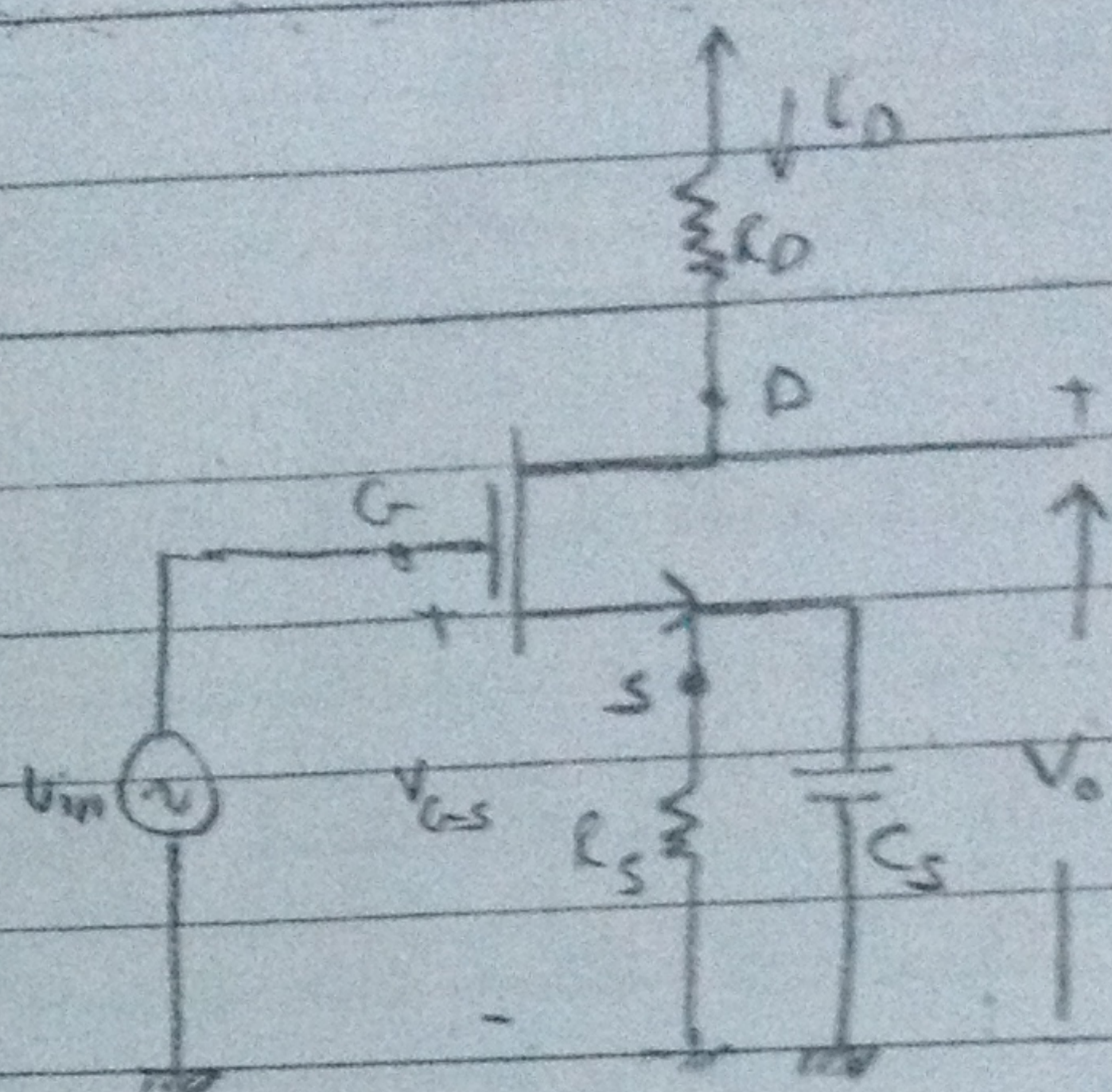


* linear equivalent model

$$v_{gs} = v_g - v_s$$

$$= v_i - 0 = v_i$$
 
$$v_o = -g_m v_{gs} \left(\frac{r_d R_D}{R_D + r_d} \right)$$



$$A_v = \frac{v_o}{v_i} = \frac{g_m r_d}{1 + r_d / R_D} = \frac{\mu}{1 + r_d / R_D}$$

(c) For a common source FET amplifier

using the high freq small signal model: the i/p admittance


$$y_i = \omega C_{gd} A_v + j\omega [C_{gs} + (1 - A_v) C_{gd}] = R_i + j\omega C_i$$

in general, A_v will be a relatively large negative number so C_i will be much larger than might be expected from the values of C_{gs} and C_{gd} . this increase in capacitance is called Miller effect, in general it is desirable for the i/p admittance to be small, therefore C_{gs} and C_{gd} should both be small during FET Fabrication, and also this effect can be diminished, if $|A_v|$ were small.


Question: 4

steps to fabricate a BJT:

 1. A lightly doped layer of n -type material is epitaxially grown on a p^+ wafer. The n -s.c. will constitute the collector material, the p^+ support can be used to provide efficient device isolation when the device is used in IC. This isolation can be achieved by applying a strong -ve bias to the p^+ s.c.
2. The wafer surface is oxidized, and using photolithographic step to create the appropriate mask, a p -layer (the base region) is diffused in the n -material.



 3. The oxide layer is stripped away and a new layer is grown, usually by wet oxidation process.
4. Using photolithography, another mask is created that exposes the s.c. material at the proper positions for diffusion of the emitter and of the collector contact regions.
5. By either diffusion or ion implantation, shallow heavily doped n and n^+ regions are fabricated, they are the emitter and ohmic contact regions of the collector.




(11)

11

the oxide layer is stripped away and a new oxide coating is grown, then using photolithography another mask is created that have wells opened in the oxide to permit contact with the various regions of the Transistor

 7. the whole face of the wafer is metallized and using another mask, the metal is etched to yield the desired electrode configuration. show in the figure below.




Question: 5

 (1) CMOS inverter

- when a HIGH is applied to the i/p, Q_1 is off and Q_2 is on, this condition connects the o/p to ground through the ^{on} resistance of Q_2 resulting in a Low o/p


- when a Low is applied to the i/p, Q_1 is on and Q_2 is off, this condition connects the o/p to $+V_{DD}$ through the ^{on} resistance of Q_1 resulting in a high o/p



this continues until the charge
 on the capacitor approaches that of a normal
 capacitor.

(12)

(ii) CMOS NAND Gate

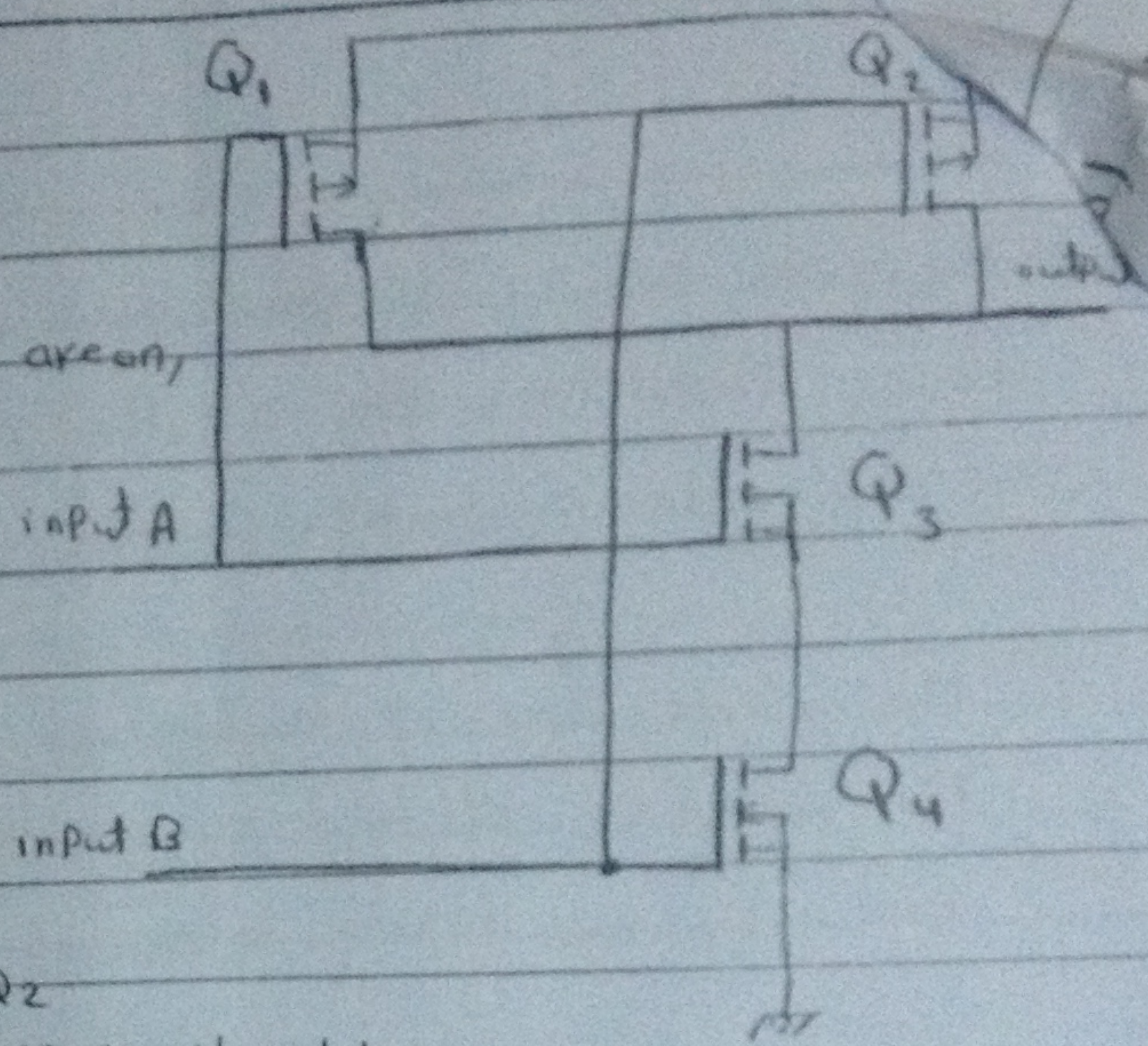

when both i/p's are low, Q_1 and Q_2 are on, and Q_3 and Q_4 are off. the o/p is pulled HIGH through the on resistance of Q_1 and Q_2 in parallel

when input A is Low and input B is HIGH, Q_1 and Q_4 are on, and Q_2 and Q_3 are off, the o/p is pulled High the low on resistance of Q_1

when input A is High and input B is low, Q_1 and Q_4 are off, and Q_2 and Q_3 are on, the o/p is pulled High through the on resistance of Q_2


finally, when both i/p's are HIGH, Q_1 and Q_2 are off, and Q_3 and Q_4 are on, in this case, the o/p is pulled Low through the on resistance of Q_3 and Q_4 in series to ground

13

15

 
(20) the unijunction Transistor:

- the UJT has a high impedance in the off state and a low impedance in the on state and is switched from one state to another by a mechanism called (conductivity modulation)



- if $I_{BB} = 0$, the I-V char is that of a usual p-n junction
- if B_2 is not left open, the I-V char are different as shown

 - For small V_E , the s.c bar has a fixed resistance $R_{BB} = R_{B1} + R_{B2}$ between B_1 and B_2



- if V_E is increased, so that V_E exceeds V_p , the emitter junction becomes forward biased and holes are injected from the p+ emitter into the n-region

- The excess holes in the n-region will tend to increase its conductivity, leading to a slight reduction in R_{B1} (this is what is known as (conductivity) modulation)

- as a result of the reduction in R_{B1} , and so the reduction of the voltage drop across it, the net forward bias across the junction increases,

- This leads to an increase in I_E , which causes further conductivity increase and so forth

- This action leads to an increase in I_E , accompanied by a decrease in V_E

this continues until the drop across R_{B1} is very small and the $I-V$ charcs approaches that of a normal p-n junction

A negative resistance region is, therefore, produced in the $I-V$ charcs after the device is switched from the off state to the on state.

Question 7


the Time width that the output is high:

$$t = 1.1(R_a)(C)$$

Let $C = 1 \text{ MF}$ and

$R_a = 5 \text{ MS}$

$$\therefore t = 5 \text{ sec}$$

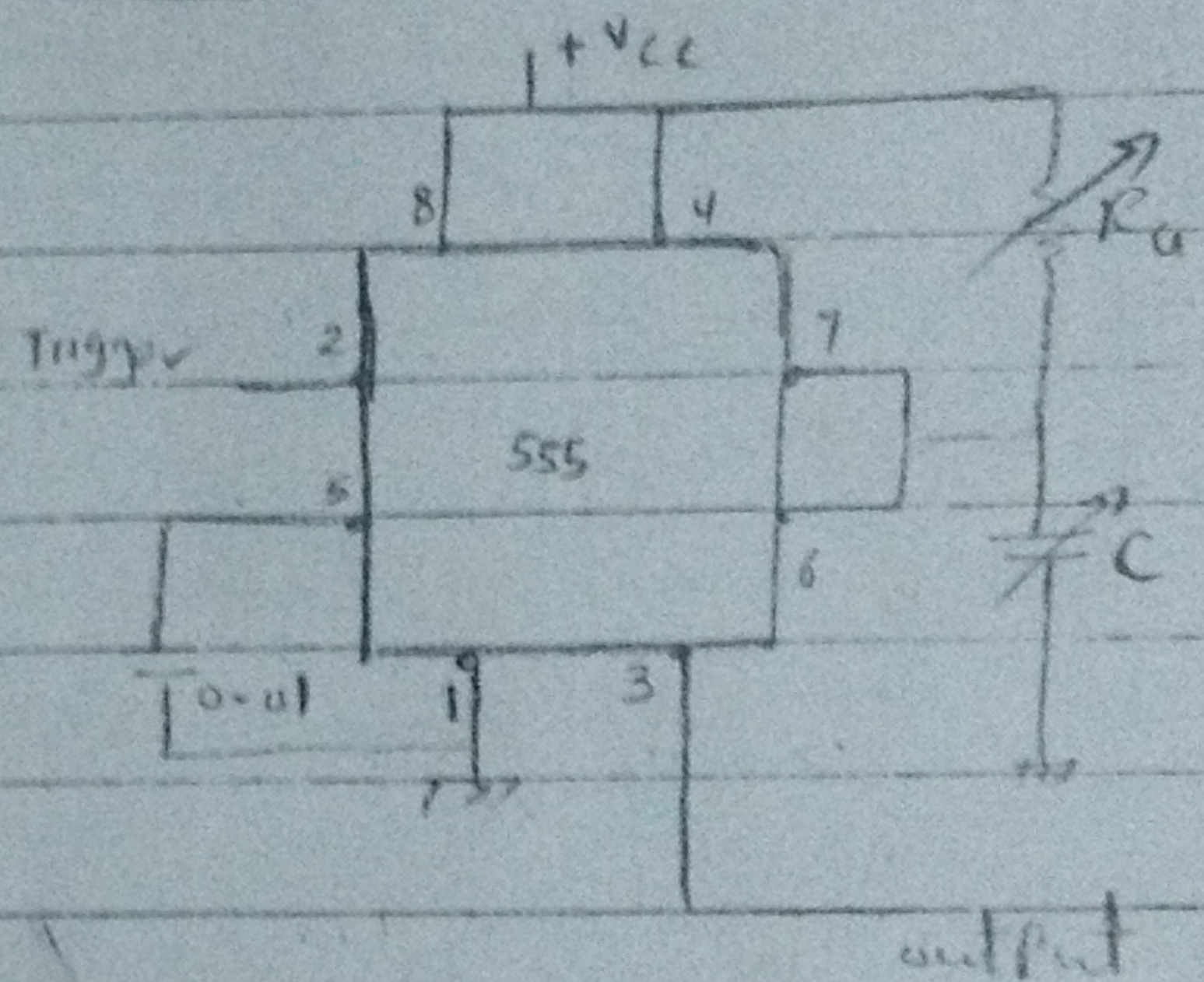

timing sequence

